


ES -116

Principles and Applications of Electrical Engineering

Semester II, 2025-26

Diode based Circuits for Different Utilities

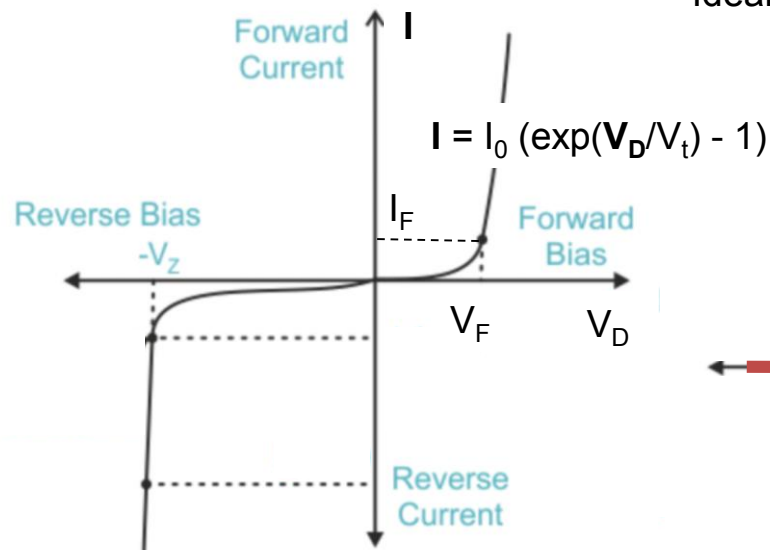
Recap: Diode Characteristics and different models




For typical silicon p-n diodes, $V_F \sim 0.7\text{-}0.9\text{ V}$ and $-V_z \sim 50\text{-}200\text{ V}$.

Specially designed Zener Diodes, $V_F \sim 0.7\text{-}0.9\text{ V}$ and $-V_z \sim 3\text{-}8\text{ V}$.

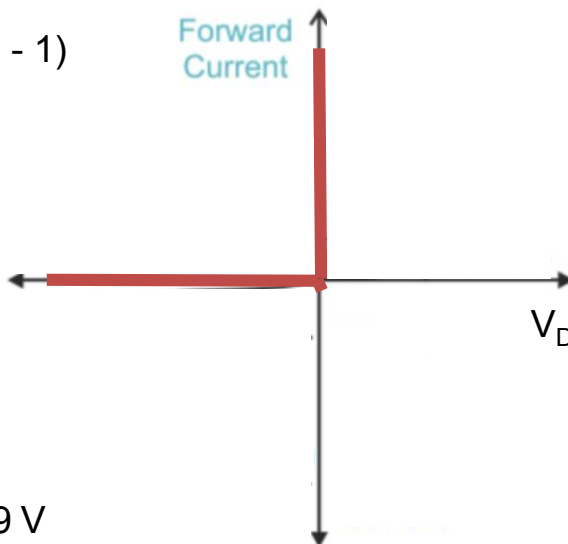
Ideal Model of the diode: Zero Drop across diode in FB



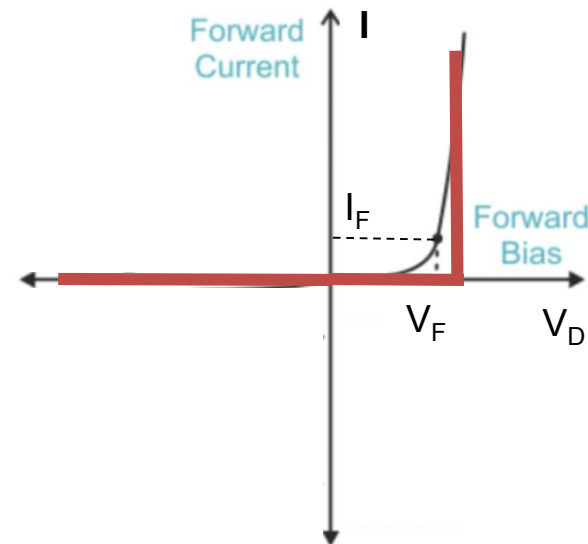More practical Model of the diode: Constant voltage Drop across diode in FB










Recap: Using constant Voltage Drop Model

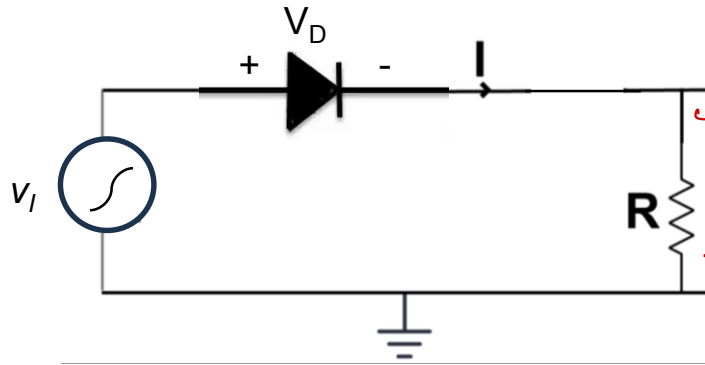


$$V_D = V_{drop} \sim 0.7 \text{ V}$$

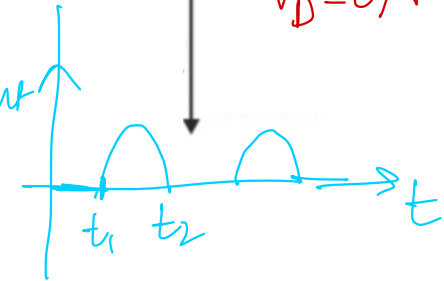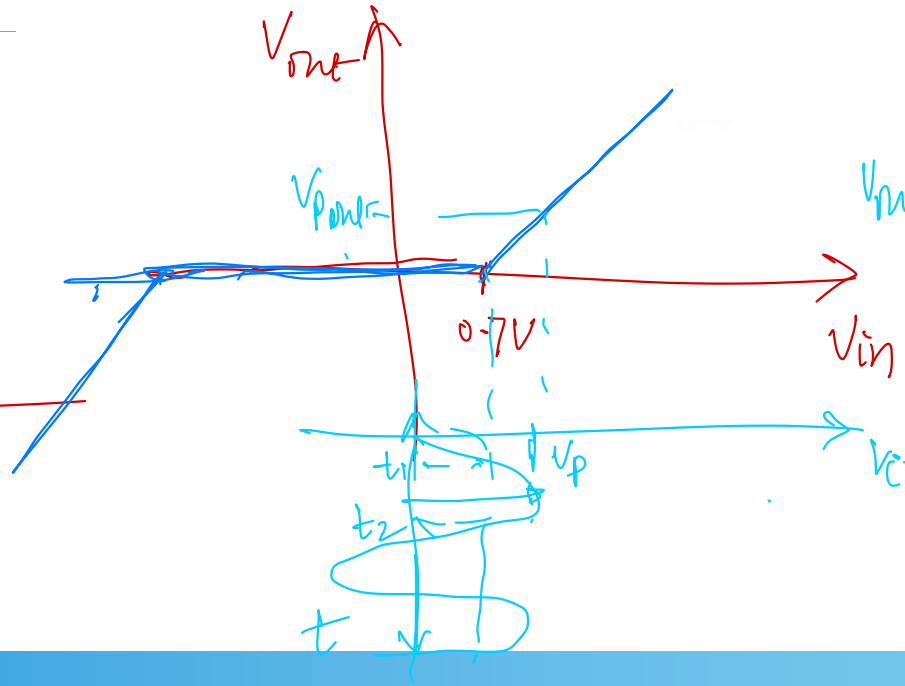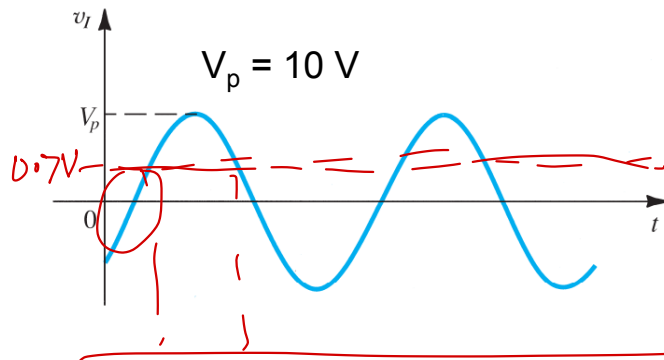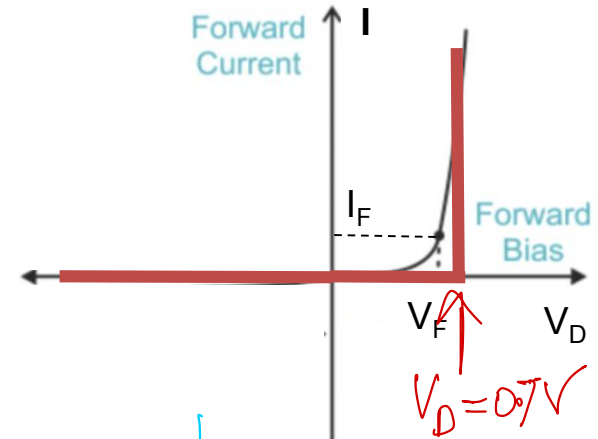Analysing the diode circuit with AC input. Calculate the output voltage across the resistor.



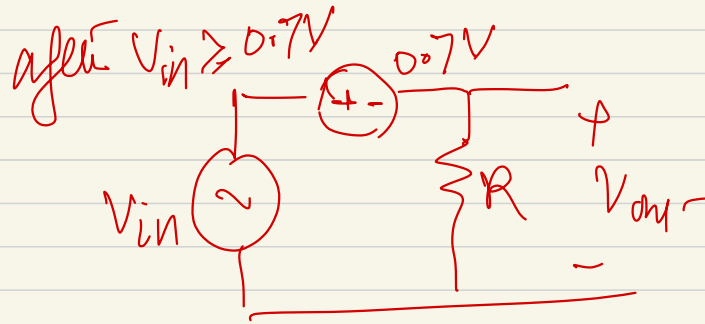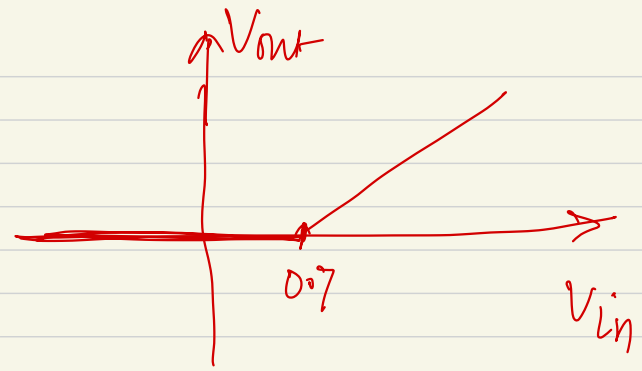
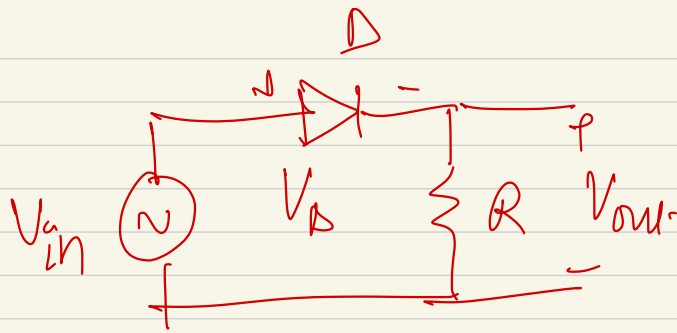


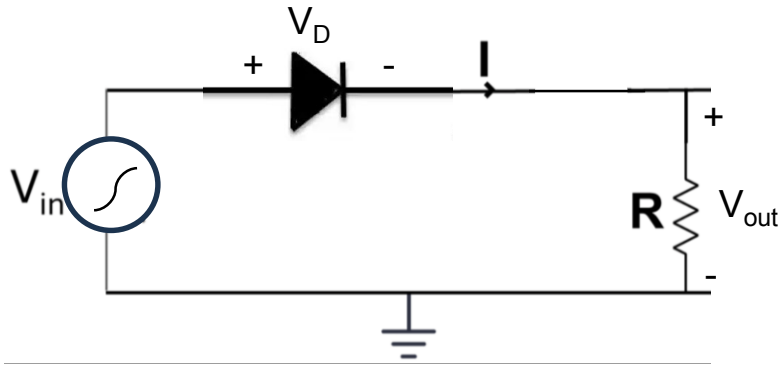Drawing Circuit's Input-Output Characteristics




$$V_D = V_{drop} \sim 0.7 \text{ V}$$

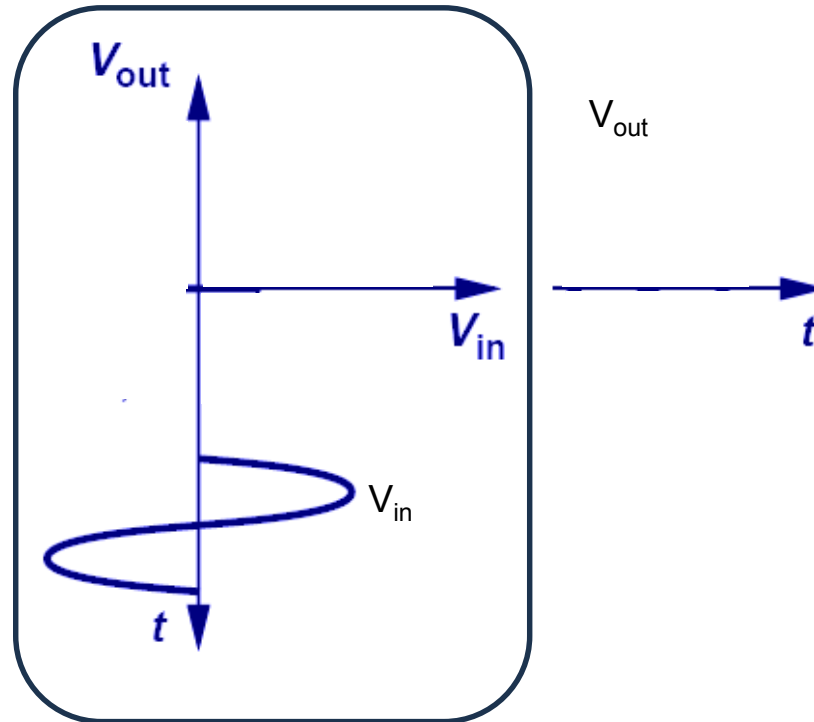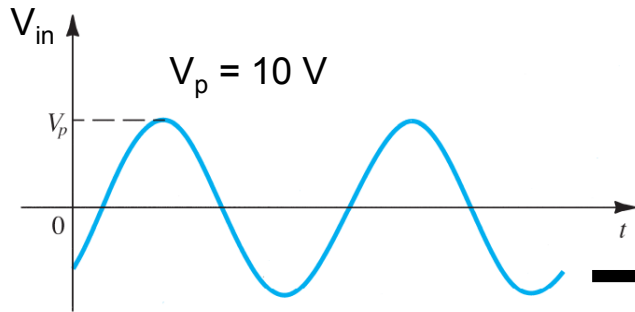Analysing the diode circuit with AC input through drawing input-output characteristics (V_{out} vs V_{in}) of the circuit




A simple application: The rectifier

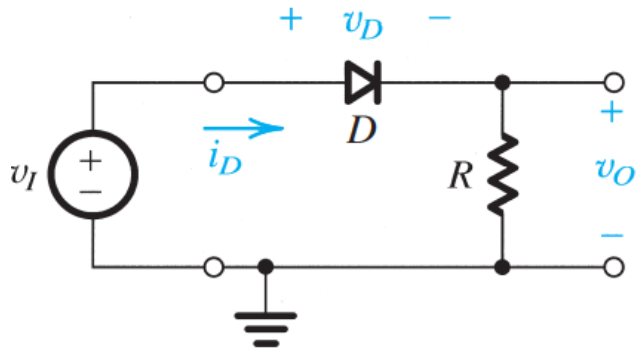

Calculate the average value of the rectified output?



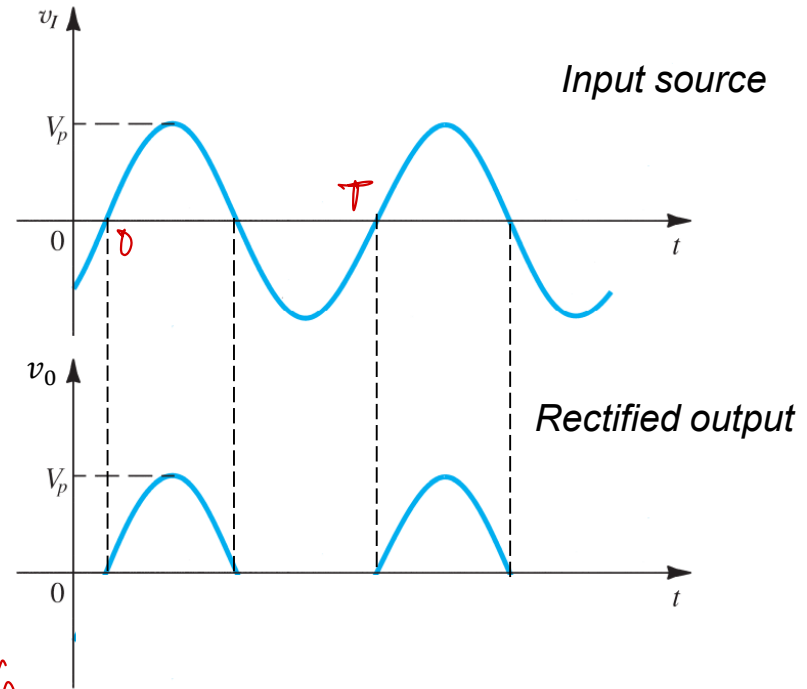
$$V_{avg} = \frac{1}{T} \int_0^T v_O(t) dt$$
$$= \frac{1}{T} \int_0^T V_p \sin \omega t dt = \frac{V_p}{\pi}$$




- **Ideal diode model** (i.e. $V_{drop} = 0$) can help us in quickly analyse circuits with diodes to understand its functionality.

Is half-wave rectifier enough?

An application: AC to DC power supply

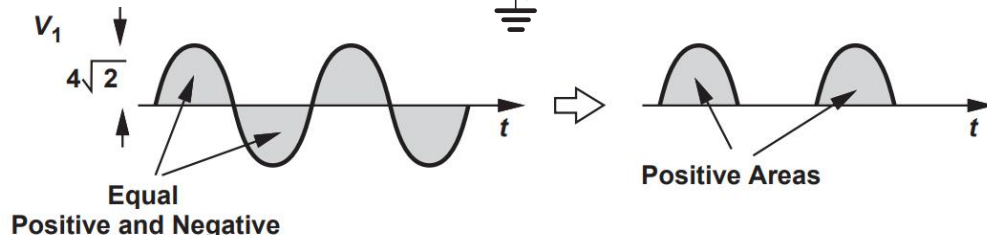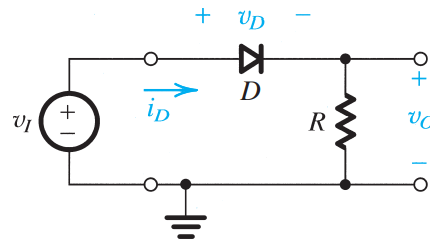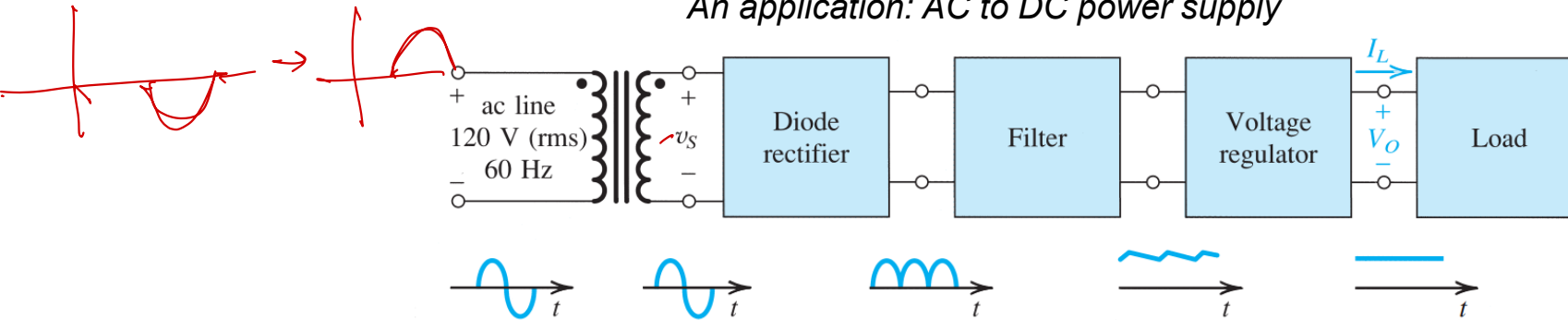


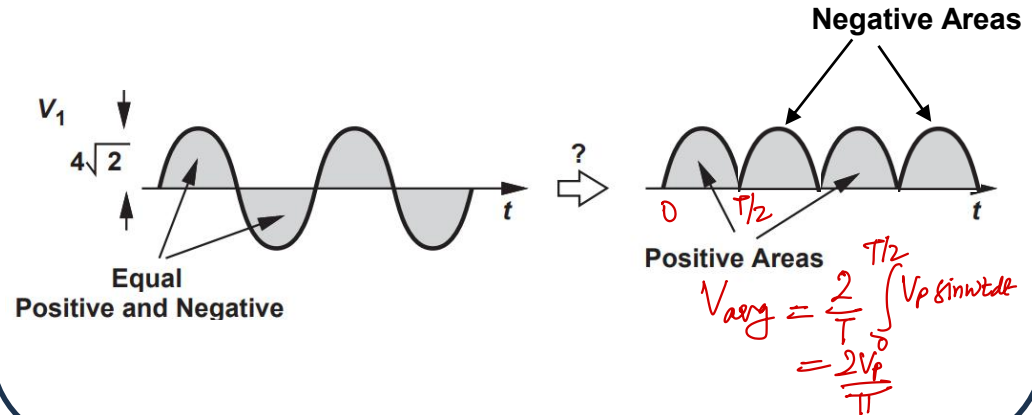Maximizing the average voltage i.e. power in the rectified signal




Practical Problem: Converting an AC to a DC





An application: AC to DC power supply

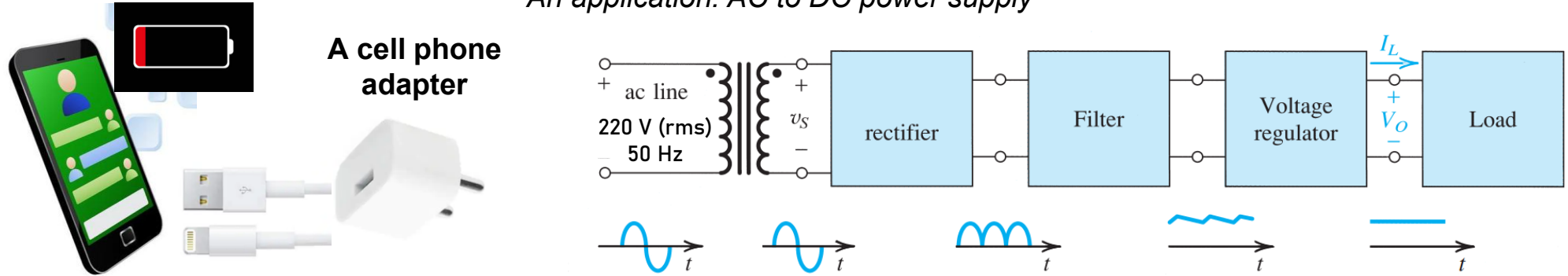




First step


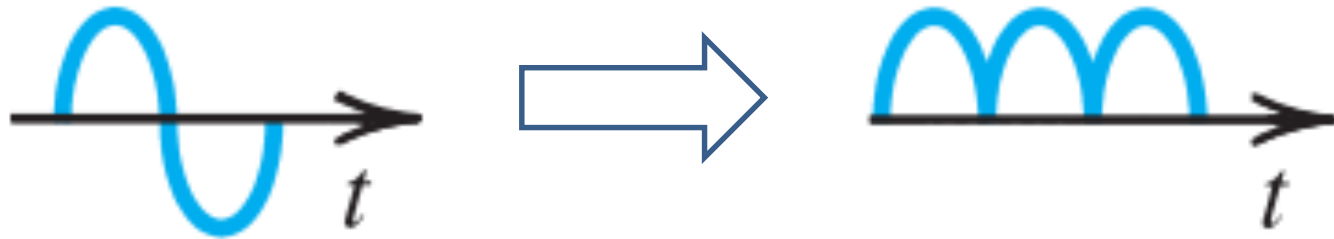


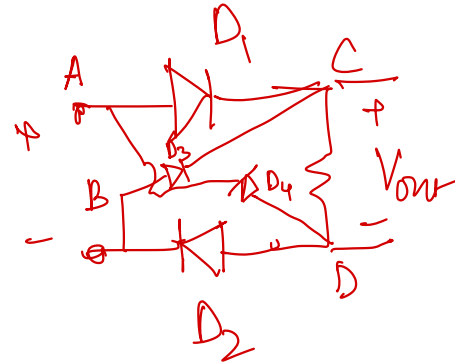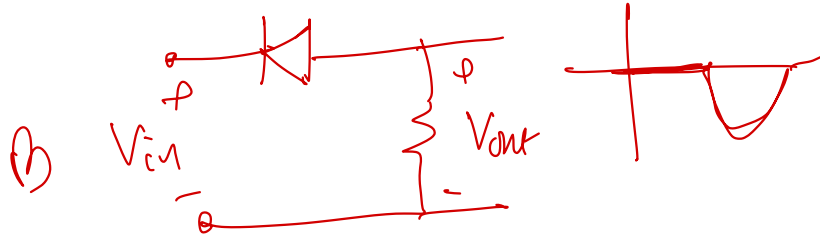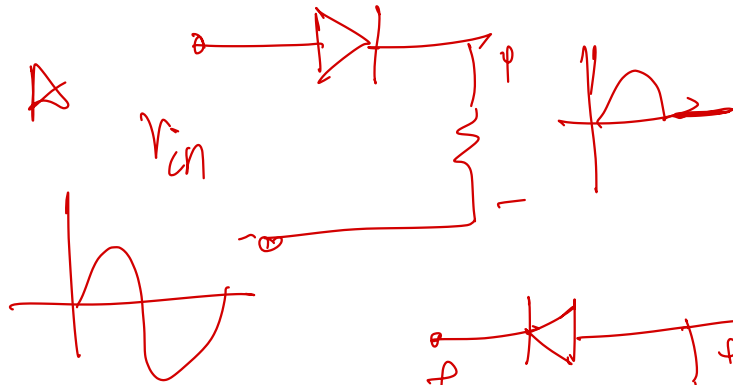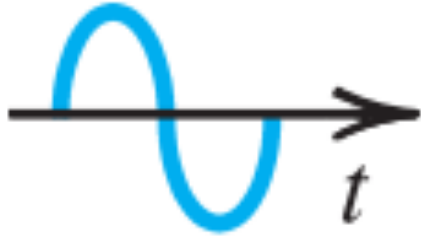How to achieve this using the diode circuit?




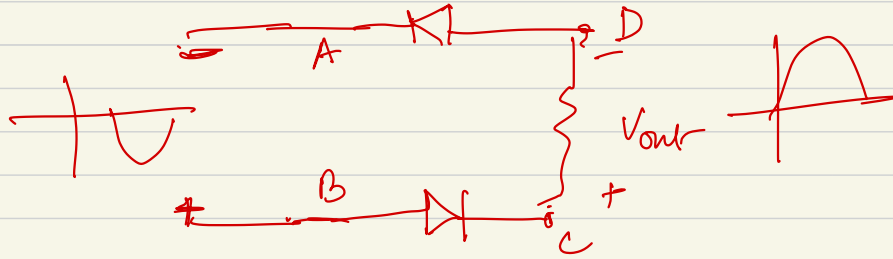
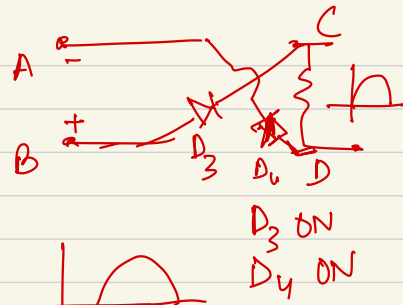
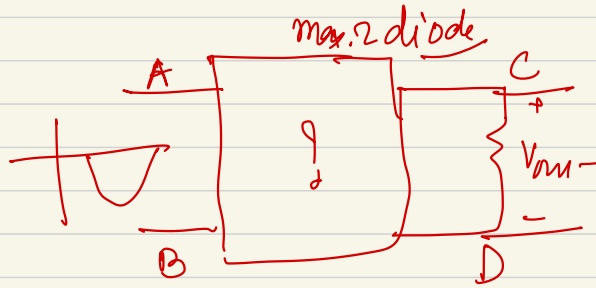
$V_{in} \rightarrow +ve$
 D_1 ON, D_2 ON
 $V_{out} \rightarrow$ 
 $V_{in} \rightarrow -ve$
 $D_1, D_2 \rightarrow OFF$



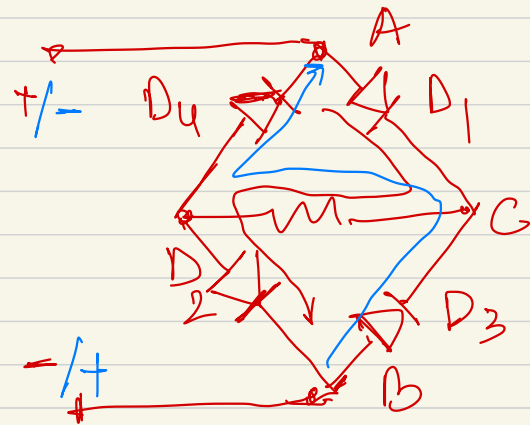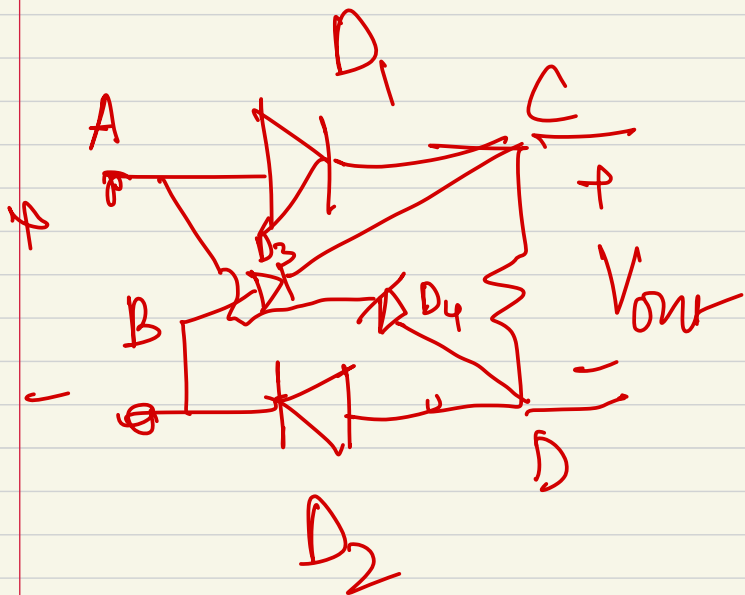


bridge rectifier

Evolution of full-wave rectifier

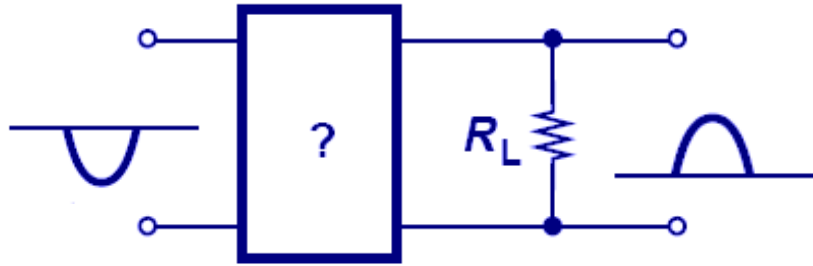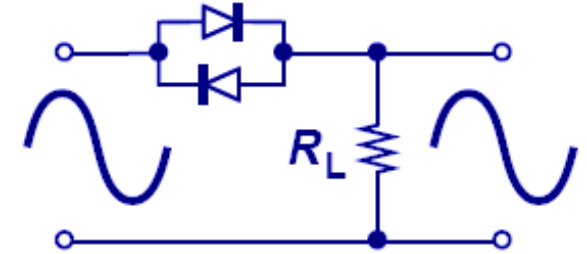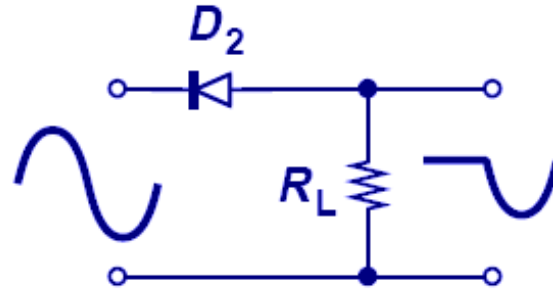
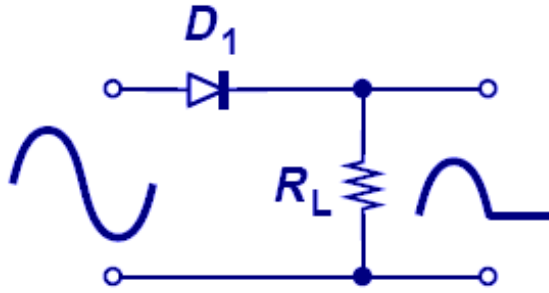


Full-wave rectifier: Bridge rectifier

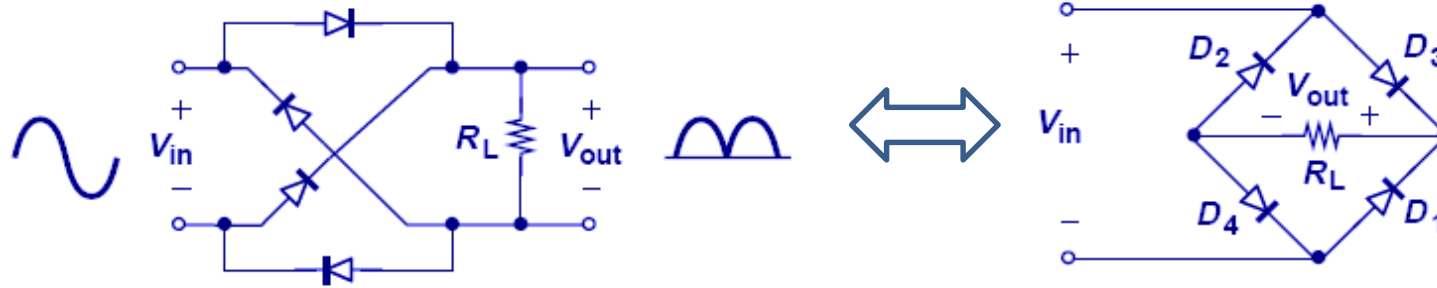





- The figure above shows a full-wave rectifier, where D_1 and D_2 pass/invert the negative half cycle of input and D_3 and D_4 pass the positive half cycle.

Full-wave rectifier: Bridge rectifier

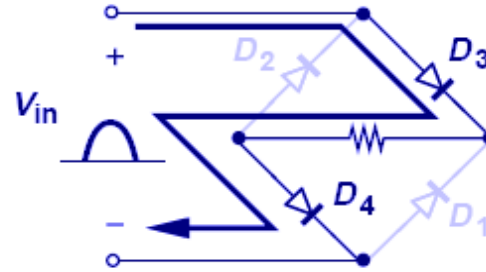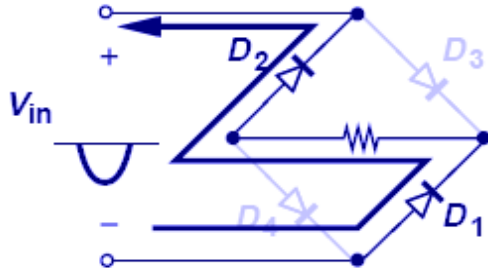



- The figure above shows a full-wave rectifier, where D_1 and D_2 pass/invert the negative half cycle of input and D_3 and D_4 pass the positive half cycle.


Next Goal

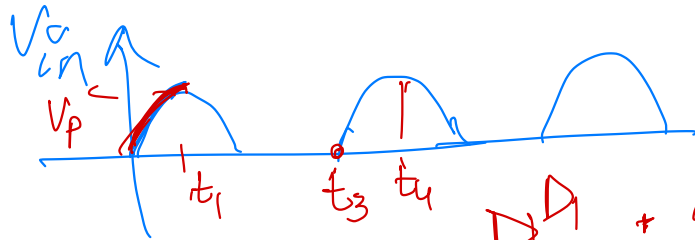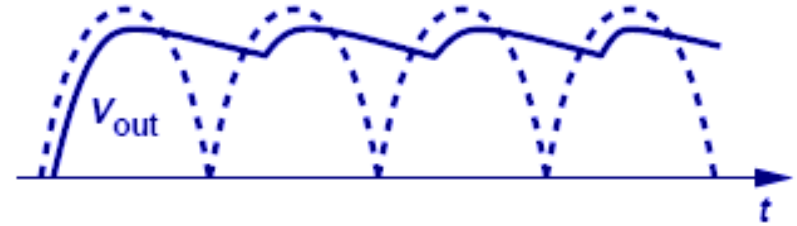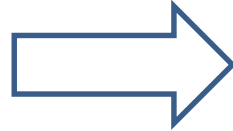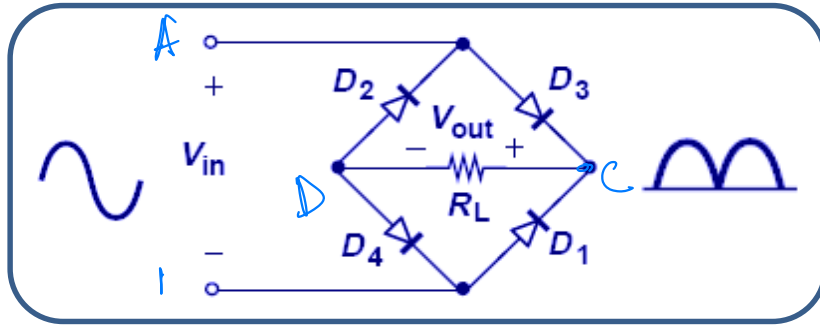




at $t = t_1 + 0^+$

$V_{D1} = -ve$
 $\rightarrow$ Off till

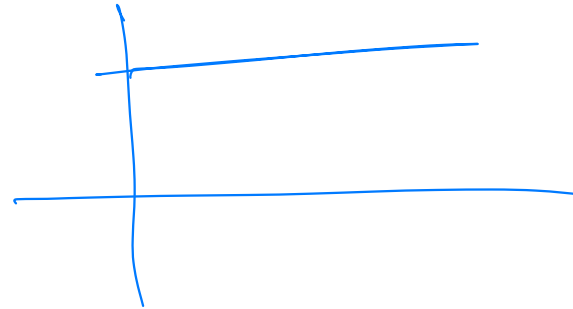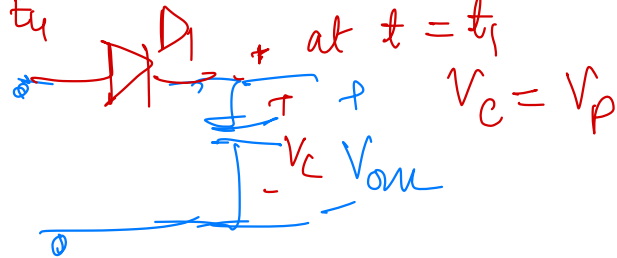


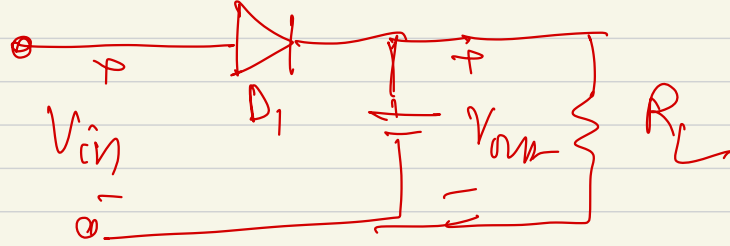


at $t = t_1 + \delta$, D_1 is off

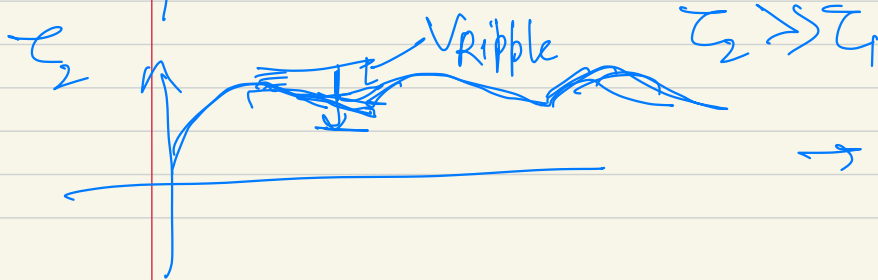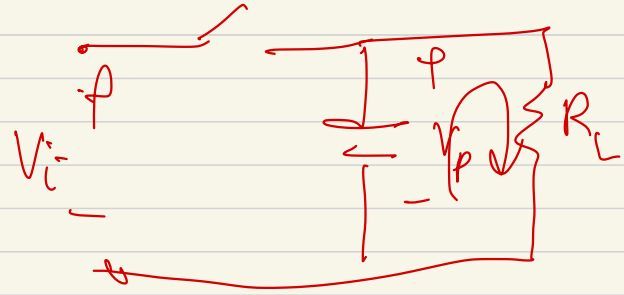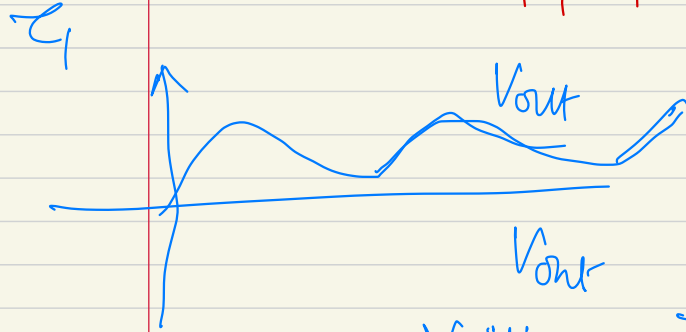


→ ripples

Diode-capacitor circuit: Ideal model

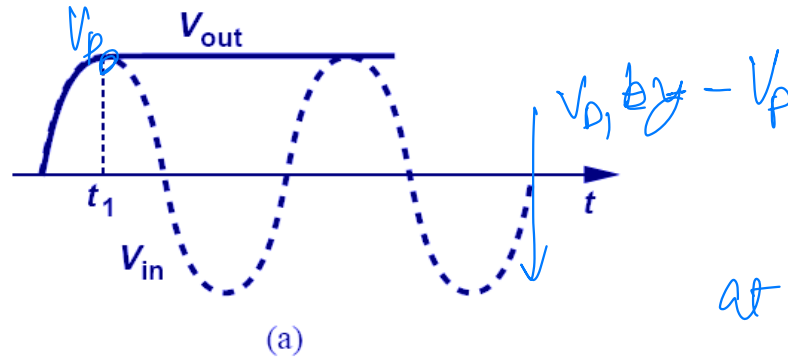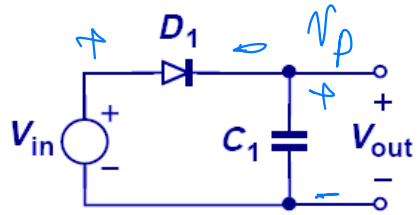


at $t = t_1$, $V_{out} = V_p$

$$V_{D1} = V_{in} - V_p$$


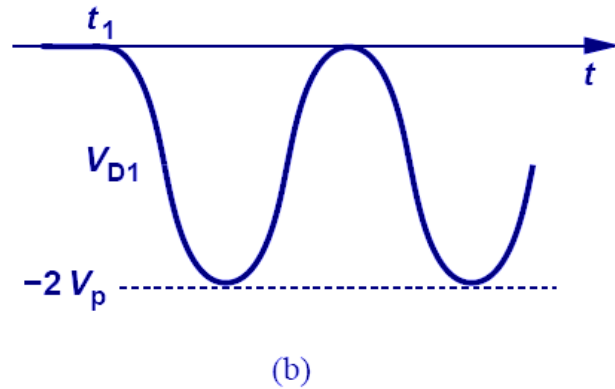


Diode-capacitor circuit: Practical model

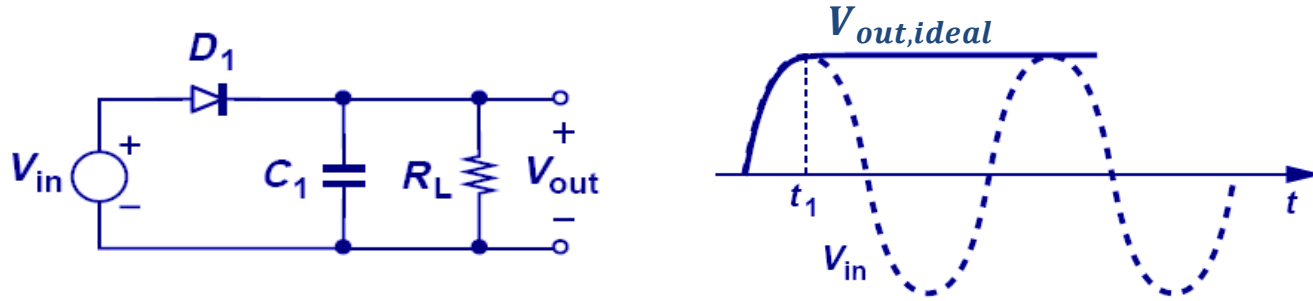

How would V_{out} look like for practical cases?

Behaviour for Different Capacitor Values

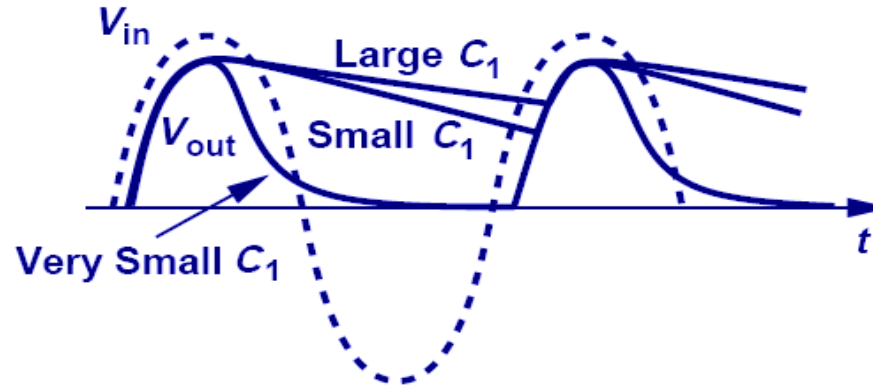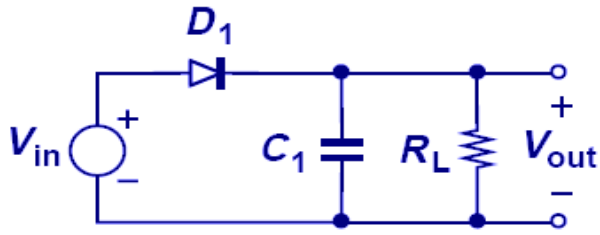

$$V_{out}(t) = (V_p - V_{D,on}) \exp \frac{-t}{R_L C_1}$$


$$0 \leq t \leq T_{in}$$

- For large C_1 , V_{out} has small ripple.



$$V_{out}(t) \approx (V_p - V_{D,on}) \left(1 - \frac{t}{R_L C_1}\right) \approx (V_p - V_{D,on}) - \frac{V_p - V_{D,on}}{R_L} \frac{t}{C_1}$$

$$V_R \approx \frac{V_p - V_{D,on}}{R_L} \cdot \frac{T_{in}}{C_1} \approx \frac{V_p - V_{D,on}}{R_L C_1 f_{in}}$$


Complete full-wave rectifier

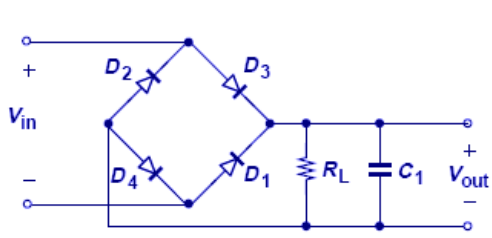
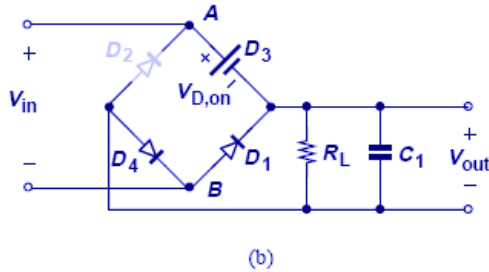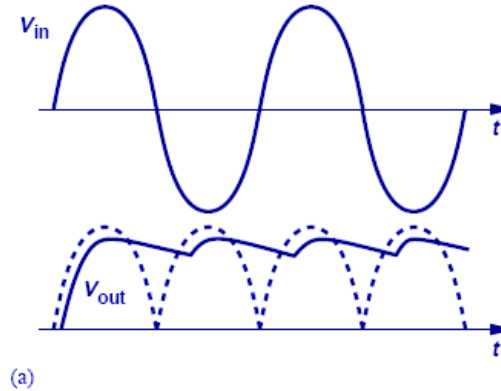
$$V_R \approx \frac{1}{2} \frac{V_P - V_{D,on}}{R_L C_1 f_{in}}$$







Current through each diode

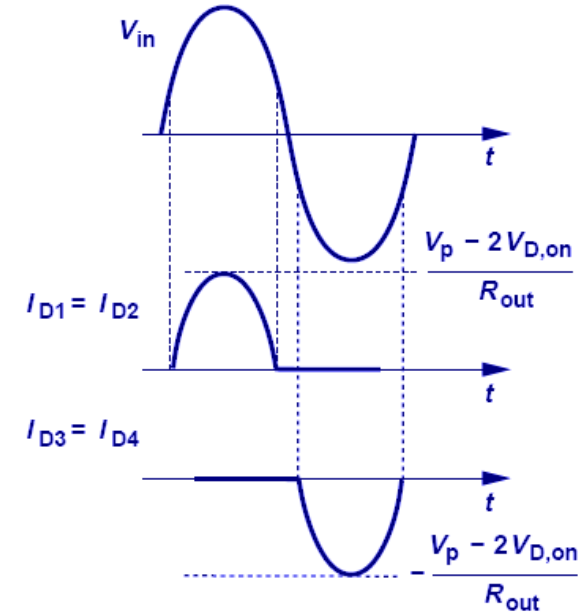

- Since C_1 only gets half of the period to discharge, ripple voltage (V_R) is decreased by a factor of 2.
- Here, each diode is subjected to approximately one V_p reverse bias drop (versus $2V_p$ in half-wave rectifier).

Half-wave vs Full-wave rectifier

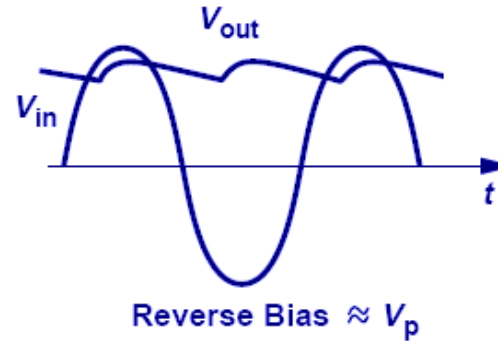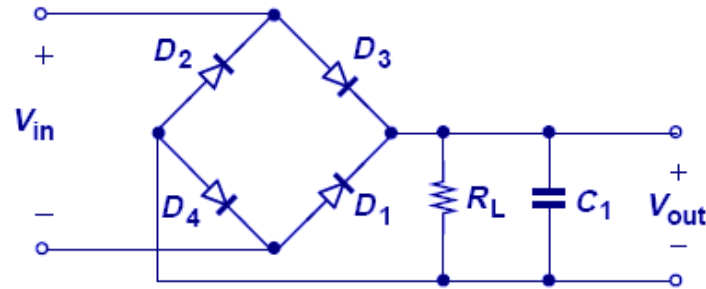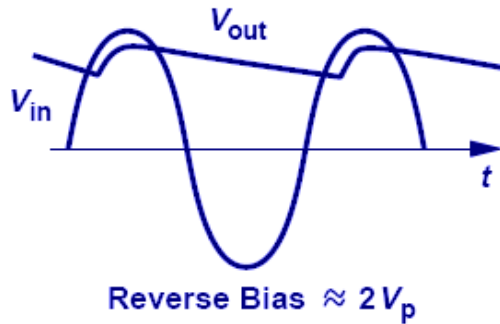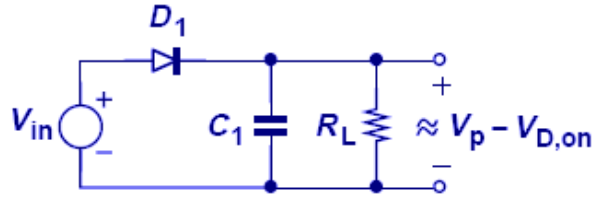


How to get rid of ripples from the rectified output?


- Full-wave rectifiers are more suited to adapter and charger applications.

Problem: Converting an AC to a DC


An application: AC to DC power supply

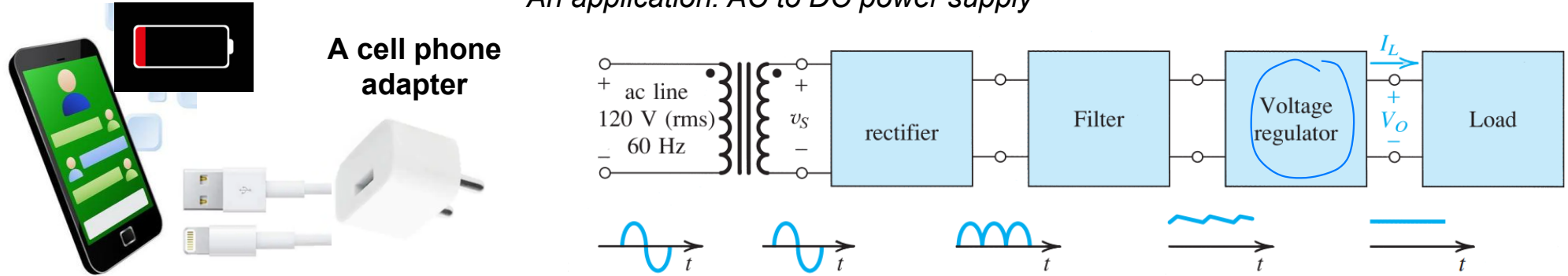

Last step

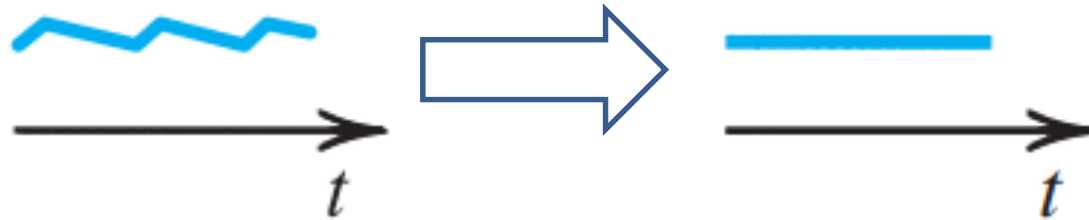

Voltage regulation with Zener diodes

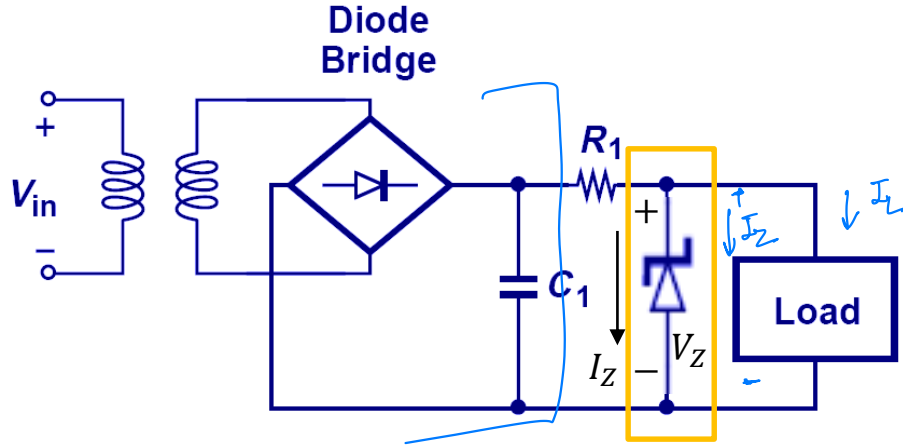

- Smaller r_d of Zener diodes in the breakdown region provides a regulated output voltage.

PRIMARY CHARACTERISTICS		
PARAMETER	VALUE	UNIT
V_Z range nom.	3.3 to 75	V
Test current I_{ZT}	3.3 to 76	mA
V_Z specification	Thermal equilibrium	
Circuit configuration	Single	

<https://www.vishay.com/docs/85816/1n4728a.pdf>



I_{ZK} : Knee current

V_{ZK} : Knee voltage

V_Z : Voltage across Zener diode at I_{ZT}

I_{ZT} : Test current specified in the data sheet


Circuit symbol of Zener diode

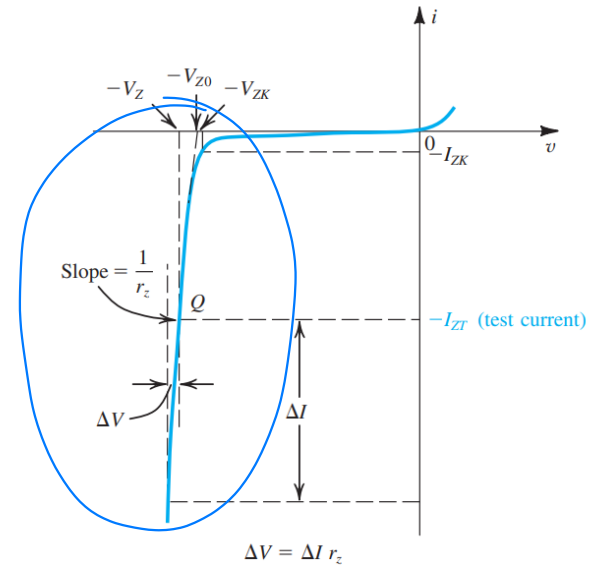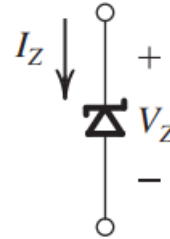

- It was introduced in the last problem of the last tutorial!

More Diode Based Circuits

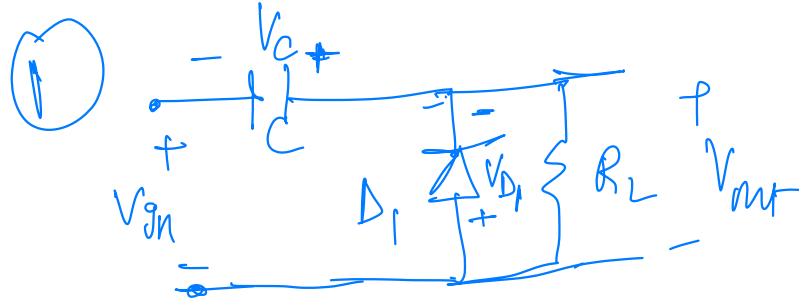- For example, practice clamper and other diode based circuits.



assume $R_L C \gg T_{in}$

-ve, $D_1 \rightarrow$ is ON till $t=t_1$
 for $t_1 < t < t_2$, $V_{D_1} < 0$ as
 V_C is +ve $\Rightarrow D_1$ is OFF


When D_1 is ON $\rightarrow V_{out} = 0$ ($t < t_1$)

When D_1 is OFF $\rightarrow V_{out} = V_{in} + V_C$

in region II, $V_{out} = V_{in} + V_C$ i.e. V_{out}

shifted by V_C (which is constant assuming very high time constant)

you have done this circuit in the lab!

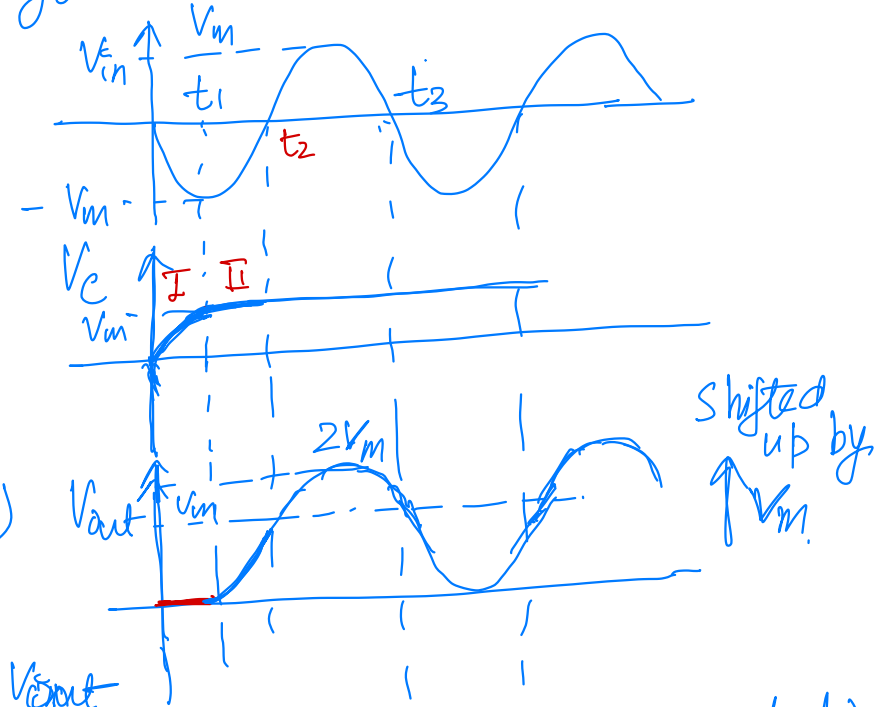

More Diode Based Circuits

- For example, practice clamper and other diode based circuits.

for $t > t_2$, when V_{in} is +ve $\rightarrow D_1$ remains OFF as $V_{D_1} < 0$
 $\Rightarrow V_{out} = V_{in} + V_C$, V_{out} shifted by V_C

for $t > t_3$ when V_{in} goes -ve, voltage across diode remains = 0, as $V_C = V_m$


D_1 remain off $\Leftarrow$ even $V_{in} = -V_m$
 $V_{out} = V_{in} + V_C$ as $V_{D_1} = -(V_{in} + V_C)$

it continues.

More Diode Based Circuits

- For example, practice clamper and other diode based circuits.

Homework

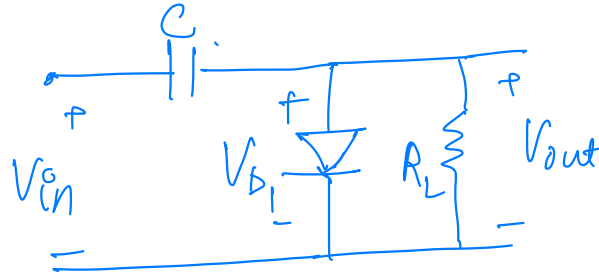

Draw V_{D1} & V_{out}
for a sinusoidal V_{in} .