

Tutorial-4 Quiz Solutions

A. For $t < 0$, switch is at a.

In steady state, $L \rightarrow S.C.$

$$i(0^-) = I_S = \frac{5}{10} = 0.5 \text{ A}$$

at $t=0$, switch flips to b.

$i(0^+) = 0.5 \text{ A}$ (due to current inertia of the inductor)


B.

$$V_L(0^+) + 10 \times 0.5 = 24 \Rightarrow V_L(0^+) = 19 \text{ V}$$


Because $i(0^-)$ dictates $V_L(0^+)$.

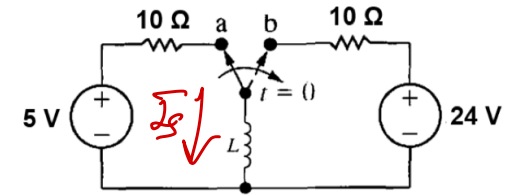Q1. You are analyzing a fuel injector solenoid. It can be modeled as a series R-L circuit ($R = 10 \Omega$, $L = 100 \text{ mH}$). Instead of a simple on/off switch, the circuit is controlled by a 2-Position Switch, as shown in the figure.

The switch has been in Position A for a long time (Steady State 1). At $t=0$, the switch instantly flips to Position B.



- Calculate the current flowing just before the switch flips, $i(0^-)$. What is the current $i(0^+)$ the exact instant the 24 V source is connected? Why doesn't the current jump to 2.4 A immediately?
- At $t=0^+$, calculate the voltage across the inductor $v_L(0^+)$ at this exact moment. How can the inductor voltage be *almost* as high as the source?
- Write the mathematical expression for $i(t)$ for $t > 0$. (Hint: Use the General Solution $i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$).
- However, the fuel injector is a mechanical valve held shut by a stiff spring. The magnetic force is only strong enough to pull the valve open once the current exceeds 1.5A. Use your equation to calculate the exact time t_{open} when the current crosses the 1.5A threshold.
- The engine control unit (ECU) needs this injector to open within 3 ms of the command signal to ensure fuel enters the cylinder at the correct moment for combustion. Does your circuit meet this specification, or is the inductor too slow?

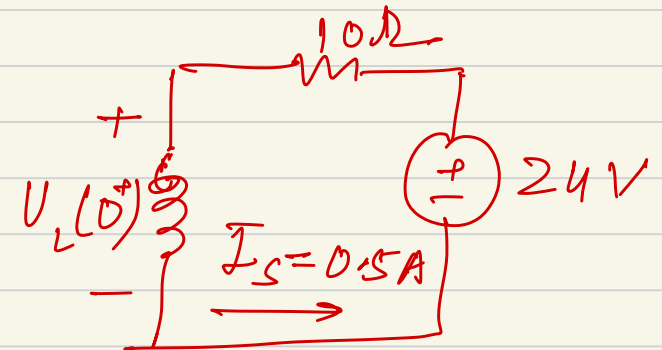

C. $i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$, $\tau = \frac{L}{R} = \frac{0.1}{10} = 0.01s = 10ms$

$i(\infty)$ can be calculated when $L \rightarrow s.c$ in 24 V loop.

$$i(\infty) = \frac{24}{10} = 2.4A$$

$$i(0) = 0.5A$$

$$i(t) = 2.4 - 1.9e^{-t \times 100}$$

D. at $t=0$, $i(0) = 0.5A$

at $t=t_{open}$, $i(t_{open}) \geq 1.5A$

$$1.5 = 2.4 - 1.9e^{-t/100} \Rightarrow -0.9 = -1.9e^{-t/0.01}$$


$$\Rightarrow \frac{0.9}{1.9} = e^{-t/0.01}$$

$$\Rightarrow \ln\left(\frac{1.9}{0.9}\right) = \frac{t}{0.01} \Rightarrow t = 0.01 \times \ln\left(\frac{1.9}{0.9}\right) \approx 7.8 ms$$

E. $t_{open} > 3ms$, your designed circuit time constant is more than required.

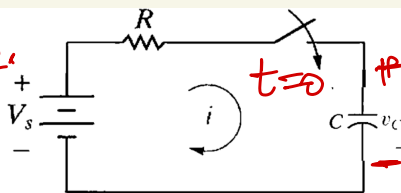Q2. You are designing the Burst Mode for a professional camera flash. The given circuit models the ~~phases~~ phase 2.

- Phase 1 ($t < 0$): When the flash fires, the voltage drops rapidly. However, the Xenon tube stops conducting (extinguishes) when the voltage drops to 50 V. It doesn't go to zero! ($v_c(0) = 50 \text{ V}$.)
- Phase 2 ($t = 0^+$): Immediately after the flash cuts off, the charging circuit activates to refill the capacitor.



$$V_s > V_c(0)$$

$$V_c(0) = 50 \text{ V}, \quad V_s = 300 \text{ V}, \quad C = 1000 \mu\text{F} \\ R = 1 \text{ k}\Omega$$

at $t = 0$, when switch closes $\rightarrow V_c(0^+) = 50 \text{ V}$ because your cap is S.C.

$$A. \quad i(0^+) = \frac{V_s - V_c(0)}{R} = \frac{300 - 50}{1 \text{ k}} = 250 \text{ mA} = 0.25 \text{ A}$$

if $V_c(0) = 0$, $i(0^+) = \frac{V_s}{R}$, it is higher than i (when $V_c(0) = 50 \text{ V}$).

$$B. \quad \text{at } t > 0, \quad V_c(t) = V(\infty) + [V(0) - V(\infty)] e^{-t/\tau}, \quad \tau = RC = 1 \text{ s}$$

Capacitor is O.C, because $V(\infty) \rightarrow V_s$

$$V(0) = 50 \text{ V} \Rightarrow V_c(t) = V_s + (50 - V_s) e^{-t/RC} \\ = 300 - 250 e^{-t}$$

A photographer takes a picture at $t < 0$. The flash fires and extinguishes, leaving the capacitor with a Residual Voltage of 50 V.

- Calculate the initial charging current $i(0^+)$ the moment the recharge begins. Does having this 50 V head start make the initial current higher or lower compared to charging from 0V?
- Write the mathematical expression for the voltage $v_c(t)$ for $t > 0$. (Hint: Use the General Solution $v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$.)
- The photographer is shooting a fast sports event and presses the shutter button again just 0.8 s after the first shot. Calculate the voltage across the capacitor at exactly $t = 0.8 \text{ s}$.
- For a "Good Exposure," the flash needs to deliver at least 15 J of energy. Did the capacitor accumulate enough energy by 0.8s to take a good photo, or will the second picture be underexposed (dark)?

C. $V_C(0.8s) = 300 - 250e^{-0.8} = 187.67 \text{ V}$

D. Energy stored in cap $= \frac{1}{2} C V_C(0.8s)^2 = \frac{1}{2} \times (187.67)^2 \times 1000 \times 10^{-6} \text{ J}$
 $\approx 17.61 \text{ J}$

if good exposure need at least 15J of energy stored in cap,
we have more than that in our cap at 0.8s $\rightarrow$ Good exposure


Q3. You are programming the motion control for the knee joint of a humanoid robot. The joint uses a high-performance Brushless Motor. One phase of the motor winding is modeled as a Resistor ($R = 4 \Omega$) and an Inductor ($L = 10 \text{ mH}$) in series. To hold a static crouched position, the motor driver synthesizes a steady sinusoidal voltage: $v(t) = 24 \sin(400 t) \text{ V}$. (Note: 400 rad/s is the electrical frequency of the drive signal).

You need to calculate the Steady State Current flowing through the winding to ensure the motor driver chip won't overheat (Limit = 4.0 A).

- Write a differential equation for this circuit in the time domain to find $i(t)$ and $v(t)$. Why is this approach considered computationally expensive for a real-time controller?
- Transform the problem into the Frequency Domain to solve it using algebra: convert the source $v(t)$ to a Phasor, and calculating the Impedance (Z_{total}), find the current Phasor Magnitude and corresponding $i(t)$.
- Based on your Phasor result, does the current exceed the 4.0 A safety limit? Why is it safe to ignore the initial startup transient when analyzing a robot holding a pose for several seconds?



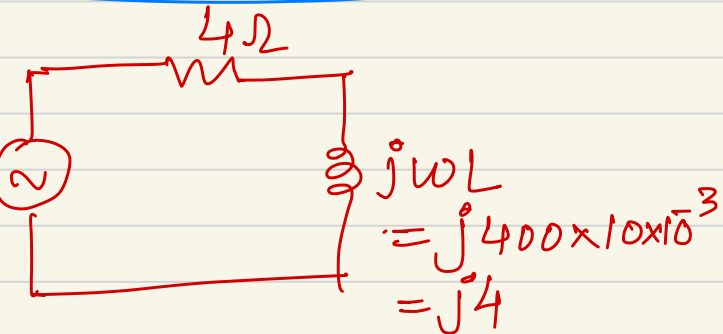In steady state $\rightarrow$ phasor domain



B. $\omega = 400 \text{ rad/s}$ $V_m \angle 0^\circ$
 $V_m = 24$

$$Z_{\text{total}} = 4 \Omega + j4 \Omega$$

$$I = \frac{24 \angle 0^\circ}{4 + j4} = \frac{24 \angle 0^\circ}{\sqrt{32} \angle \tan^{-1} 1} = \frac{24}{\sqrt{32}} \angle -45^\circ = 4.24 \angle -45^\circ$$

$$i(t) = 4.24 \cos(400t - 45^\circ)$$


C. yes, it is exceeding 4.0 A safety limit.

R-L circuit $\hat{i}(t) = \underbrace{\text{transient output term}}_{\propto e^{-R/Lt}} + \underbrace{\text{sinusoidal term}}_{\cos(\omega t + \phi - \theta)}$

for transient, calculate $\tau = \frac{L}{R} = \frac{10 \times 10^{-3}}{4} = 2.5 \text{ ms}$

$2\pi f = 400 \Rightarrow f = \frac{200}{\pi} \sim 637 \text{ Hz}$

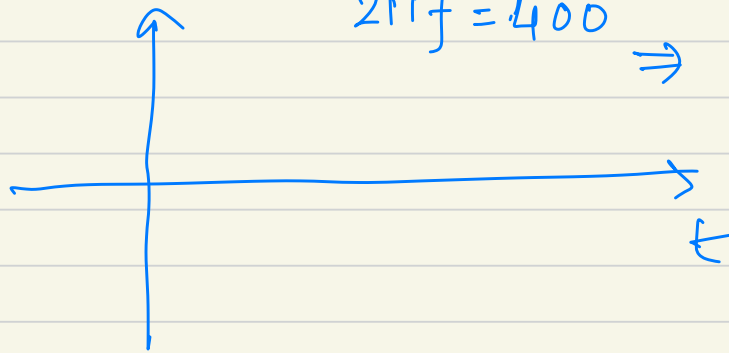
$T \approx \frac{1}{f} \sim 0.0157 \text{ s} \approx 15.7 \text{ ms}$




if the robot is holding the pose for several seconds $\rightarrow$ steady state response
should dictate the response of the circuit.

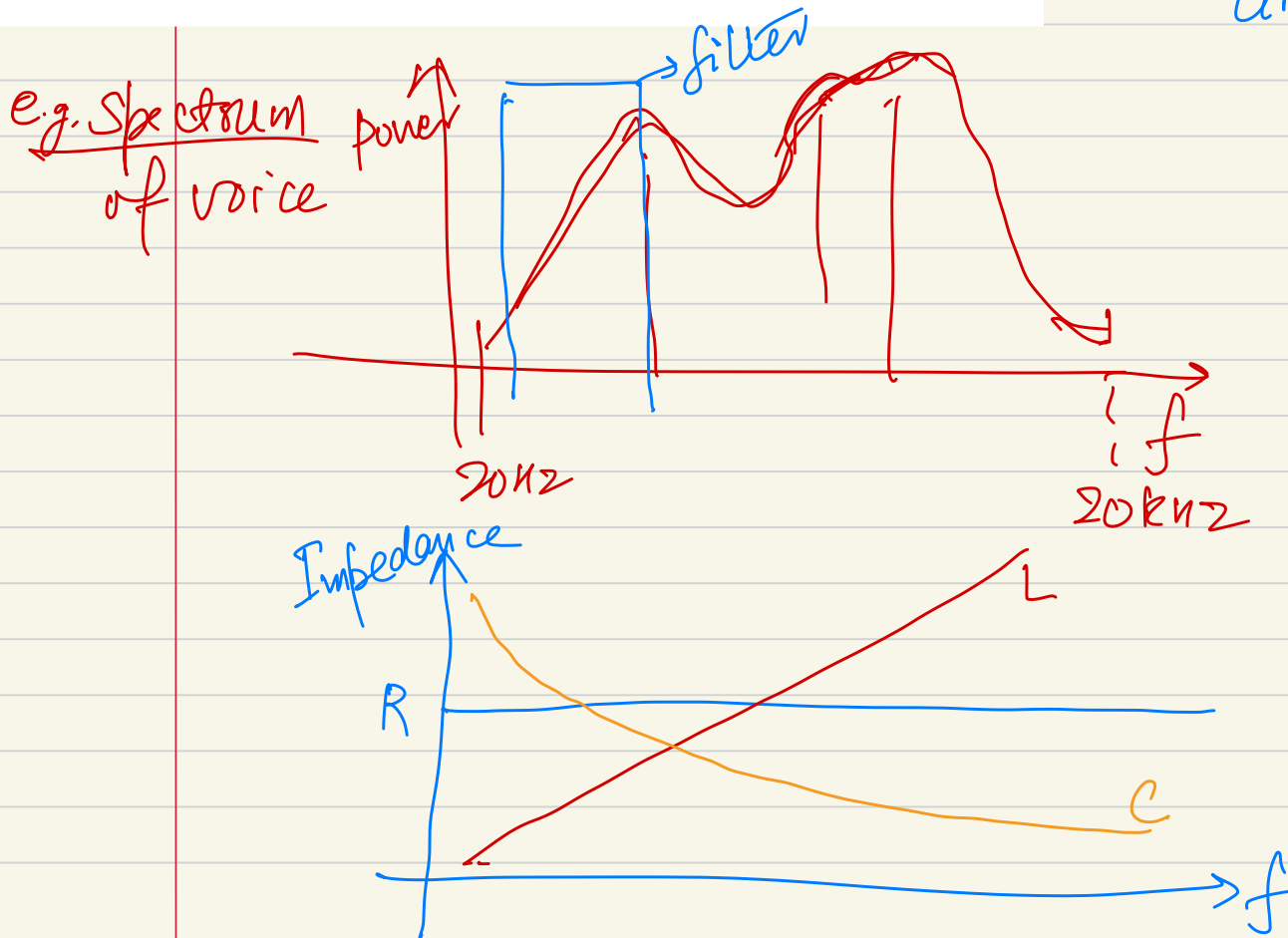Q4. You are building an analog Noise Filter for the robot's voice recognition microphone. The robot works in a noisy environment (humming servers and hissing steam). You need a circuit that blocks low rumble and high hiss, but passes the human voice clearly. Based on your friend's advice you use a series R-L-C circuit, where $R = 100\ \Omega$ representing the Output/ADC input impedance), $L = 10\text{ mH}$, and $C = 1\ \mu\text{F}$. Input is a microphone signal V_{in} containing many different frequencies.


- At very low frequencies ($\omega \rightarrow 0$), how does the capacitor act like (a short circuit or an open circuit)? Will the low-frequency rumble get through to the resistor?
- At very high frequencies ($\omega \rightarrow \infty$), how does the inductor act like (a short circuit or an open circuit)? Will the high-frequency hiss get through?



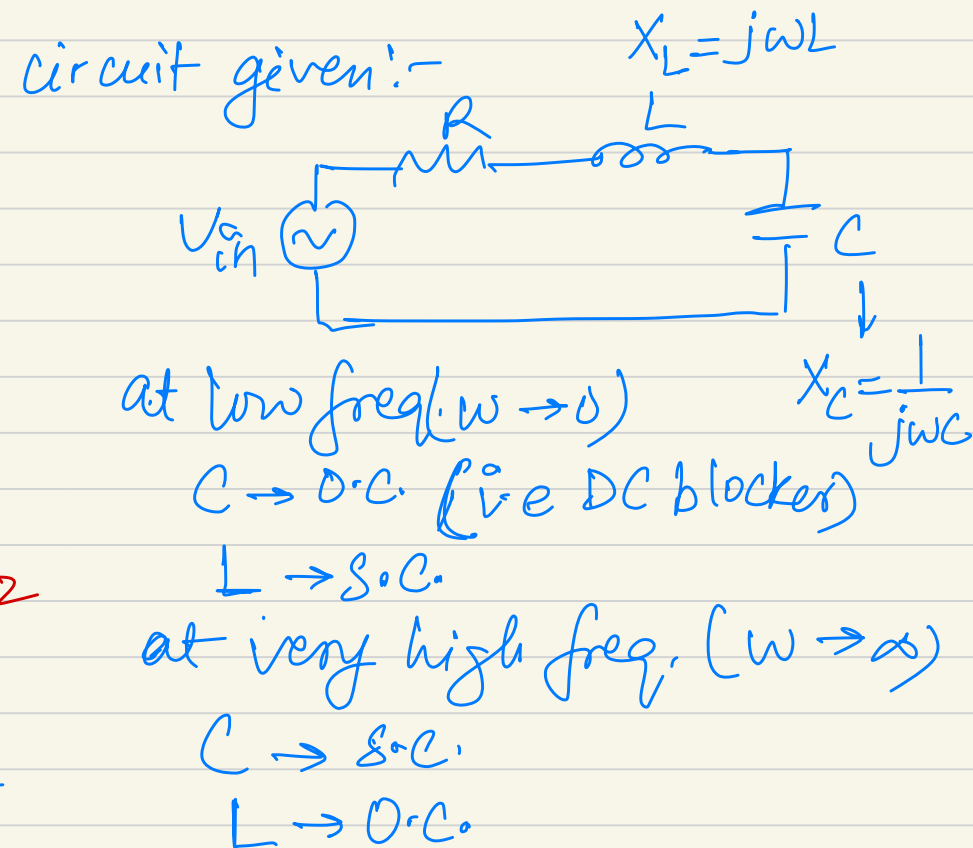- Can the Inductor and Capacitor Reactances effectively cancel each other out at specific frequency? If yes, calculate that frequency.
- Does the circuit allow maximum or minimum current at this frequency?
- If you wanted to make the filter sharper (listening *only* to a specific tone and rejecting everything else aggressively), would you increase or decrease the Resistance R ?



If output is taken across C

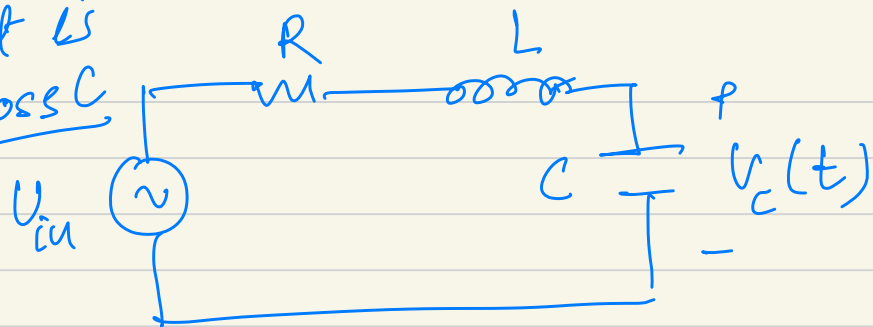


at $\omega \rightarrow 0$, $i \rightarrow 0$

$$V_C(t) \Rightarrow V_{in}$$

at $\omega \rightarrow \infty$, $i \rightarrow 0$ (b/c L is o.c.)

$$V_C(t) \rightarrow 0$$

if output is taken across R

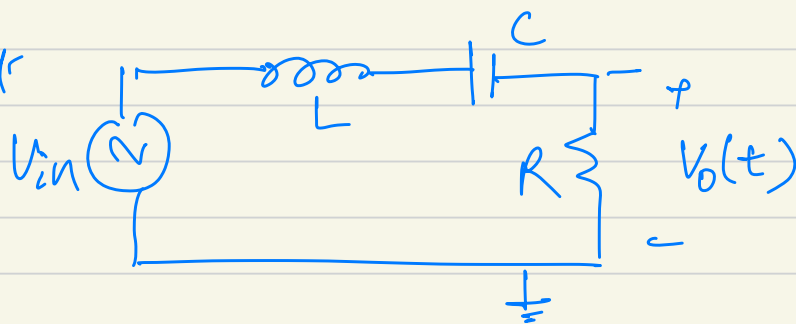

at $\omega \rightarrow 0$
Cap is o.c.


$$V_O(t) \Rightarrow 0$$

at $\omega \rightarrow \infty$, $i \rightarrow 0$ (b/c L is o.c.)

$$V_O(t) \rightarrow 0$$

$$0 < \omega < \infty$$

Impedance (Z)

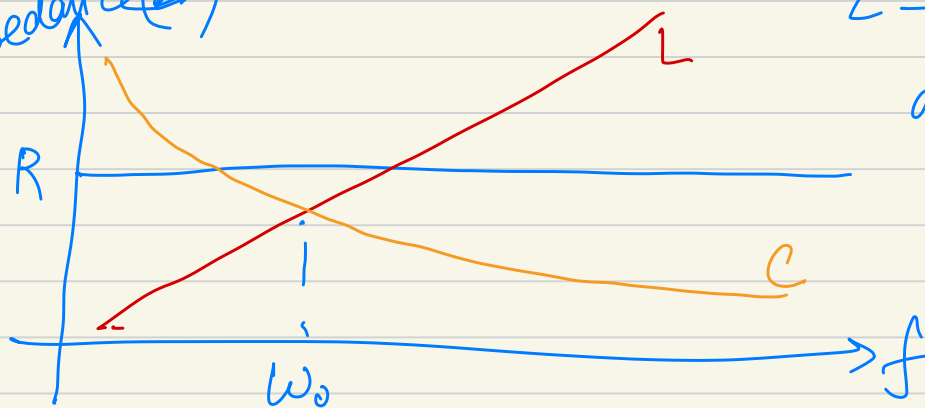

$$Z = R + j\omega L - j\frac{1}{\omega C}$$

$$\text{at } \omega_0, \quad \omega_0 L = \frac{1}{\omega_0 C} \quad (\text{i.e. } X_L = X_C)$$



$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\underline{Z(\omega_0) = R}$$

for $0 < \omega < \infty$,
$$I = \frac{V_m}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} \angle \tan^{-1}\left(\frac{\omega L - 1/\omega C}{R}\right)$$


$$|I| = \frac{V_m \cdot \omega C}{\sqrt{(\omega C R)^2 + (\omega^2 L C - 1)^2}}$$

$$\omega^2 L C > 1, |I| < I_m$$

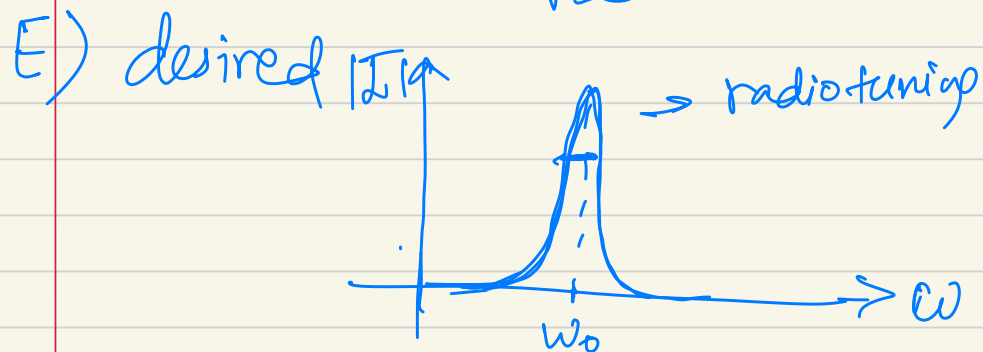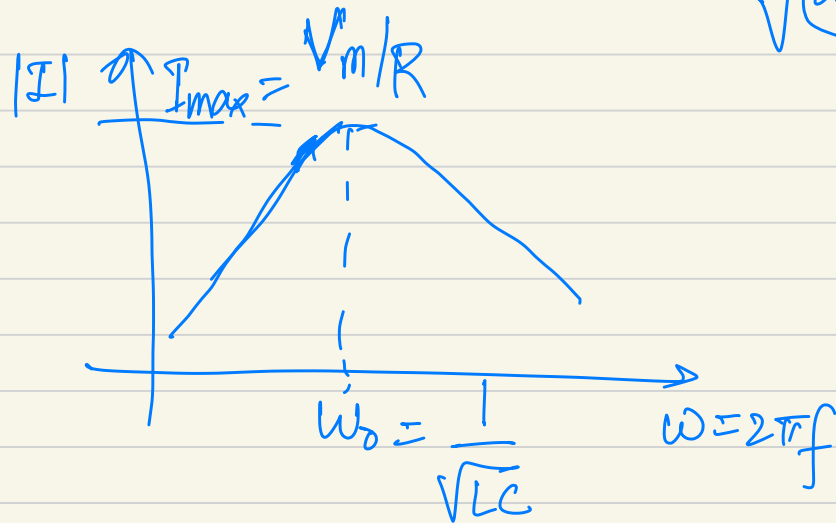

If $R \rightarrow 0$, $|I| = \frac{V_m \cdot \omega C}{(\omega^2 L C - 1)}$

practically if $\omega = \omega_0$, $|I| \rightarrow \infty$
 $\rightarrow R$ is finite due to inductor series resistance/wire resistance.

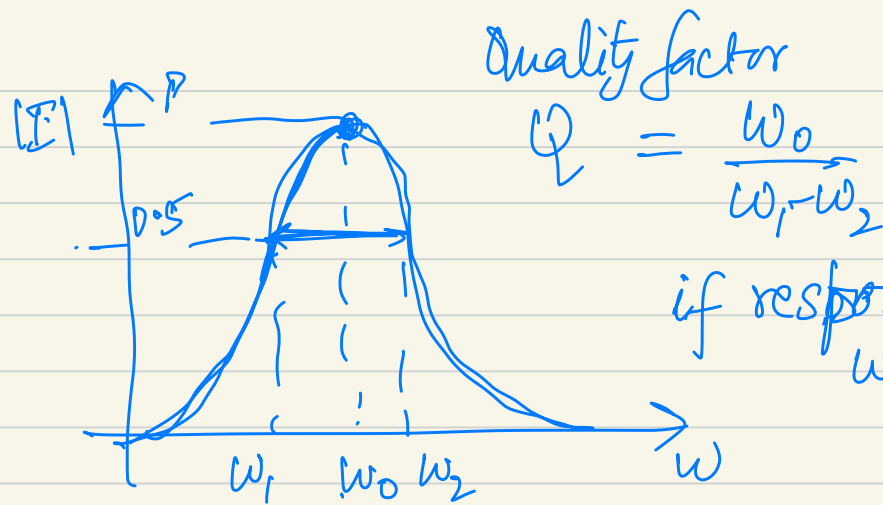

if response was close to impulse ($R \rightarrow 0$)
 $\omega_1 - \omega_2 \rightarrow 0$, $Q \rightarrow \infty$